

4

3

Full-wave Rectifier & 3-Phase Rectifier $AC \rightarrow DC$

4.1




0
(Ripple)

(Bridge Rectifier)

(Center- tapped transformer rectifier)


4.2

:

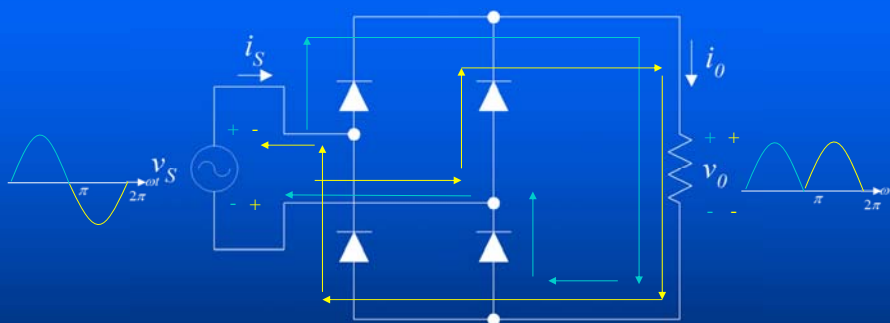


4.2

:

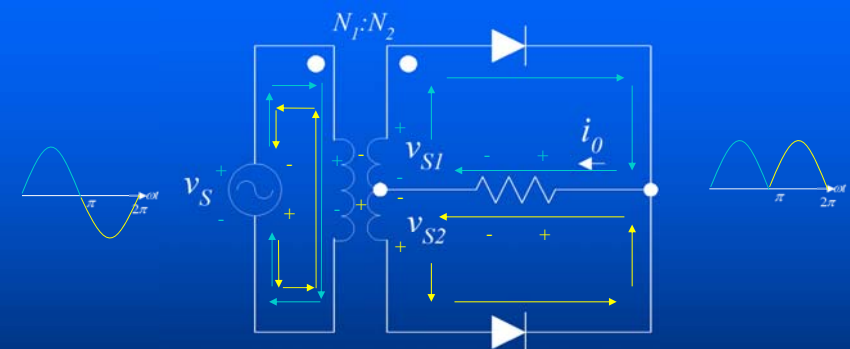


■ 양방향으로 전류가 흐름

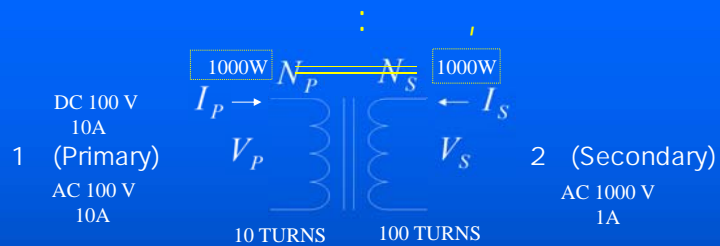

$$V_P = N_P \frac{d\phi}{dt}, V_S = N_S \frac{d\phi}{dt}, \therefore \frac{V_P}{V_S} = \frac{N_P}{N_S} \frac{d\phi}{dt} = \frac{N_P}{N_S}$$
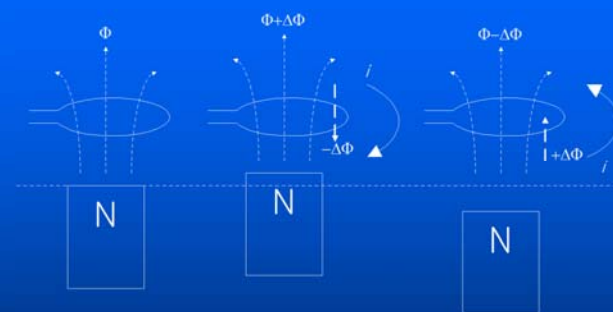
$$\frac{N_P}{N_S} = \frac{V_P}{V_S} = \frac{I_S}{I_P} = a \quad \therefore V_P I_P = V_S I_S$$



■ Faraday's Law()



$$emf = - \frac{d\phi}{dt}$$

Lentz's Law

emf: electromotive force

4.2

: R

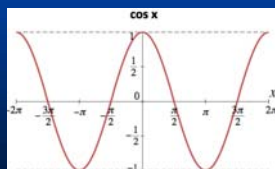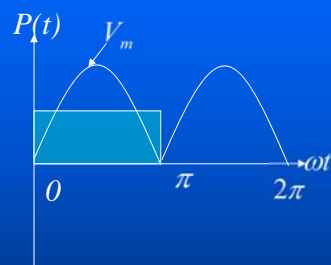

$$V_0 = \frac{1}{T} \int_{t_0}^{t_0+T} v(t) dt$$

$$V_0 = \frac{1}{\pi} \int_0^\pi V_m \sin \omega t d(\omega t)$$


$$= \frac{V_m}{\pi} [-\cos \omega t]_0^\pi \quad \int \sin dt = -\cos t$$

$$= \frac{V_m}{\pi} (-\cos \pi + \cos 0)$$

$$= \frac{2V_m}{\pi}$$

4.2

: R

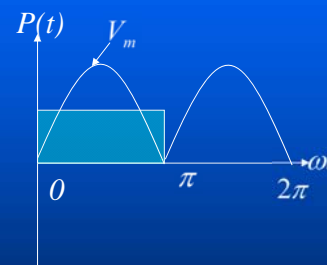

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^\pi (V_m \sin \omega t)^2 d(\omega t)}$$


$$\left[\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2} \right]$$

$$= \sqrt{\frac{V_m^2}{\pi} \left[\frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right]_0^\pi}$$

$$= \sqrt{\frac{V_m^2}{\pi} \left(\frac{\pi}{2} - \frac{\sin 2\pi}{4} - \frac{0}{2} + \frac{\sin 0}{4} \right)}$$

$$= \frac{V_m}{\sqrt{2}}$$


4.2 : R-L

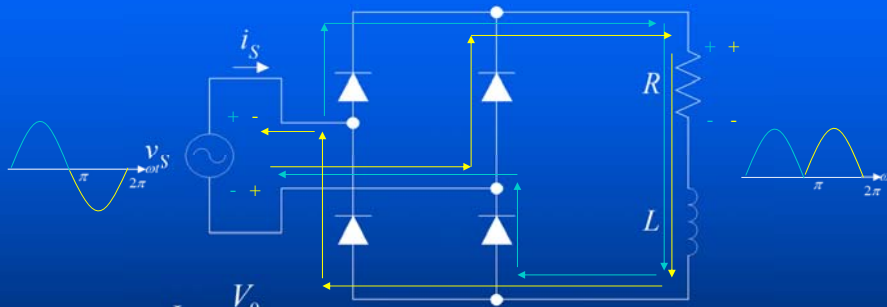

$$I_0 = \frac{V_0}{R}$$

$$I_n = \frac{V_n}{Z_n} = \frac{V_n}{|R + jn\omega L|}$$

4-2 R-L

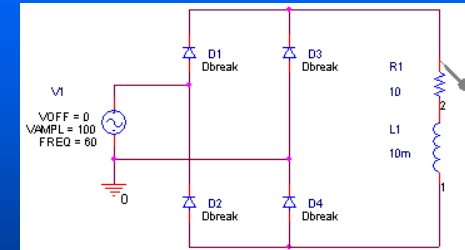


Parameter

- ✓ $R=10 \Omega$
- ✓ $L=10 \text{ mH}$
- ✓ $f=60 \text{ Hz}$
- ✓ $V_m=100 \text{ V}$
- ✓ Transient Step
=0 50 ms


Find

- ✓ I, I_{avg}, I_{rms}

4.2 :R-L

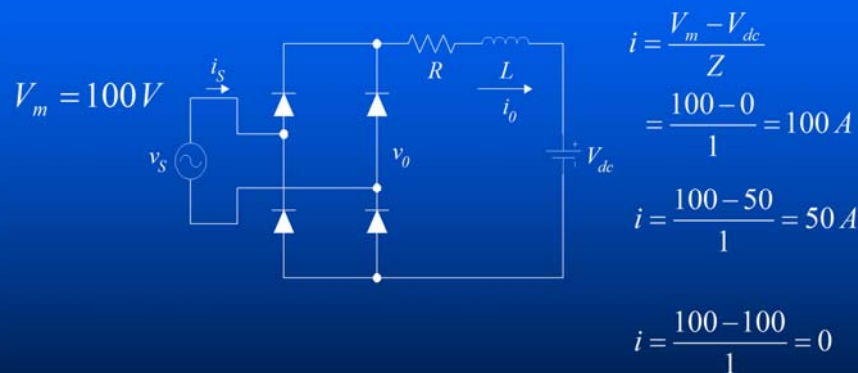

4-3 R-L

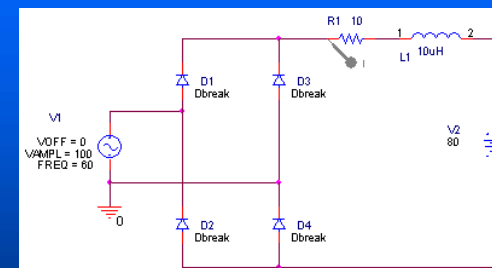

Parameter


- ✓ $R=2 \Omega$
- ✓ $L=10 \text{ mH}$
- ✓ $f=60 \text{ Hz}$
- ✓ $V_m=100 \text{ V}$
- ✓ $V_{dc}=80 \text{ V}$
- ✓ Transient Step
=0 50 ms

Find

- ✓ P, I_{avg}, I_{rms}


4.2

: R-C

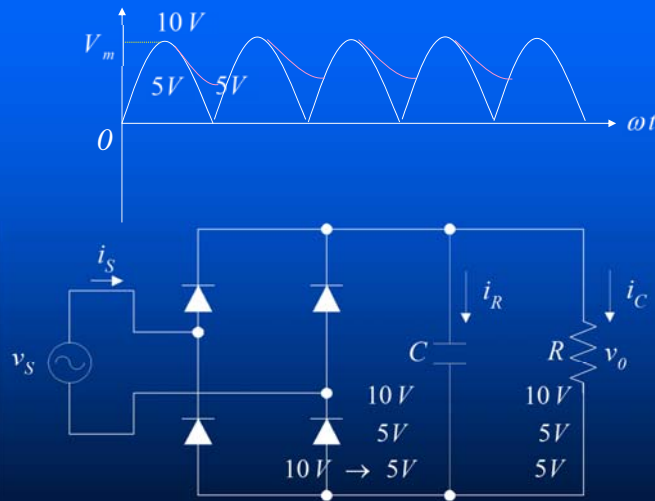

4.2

: R-C

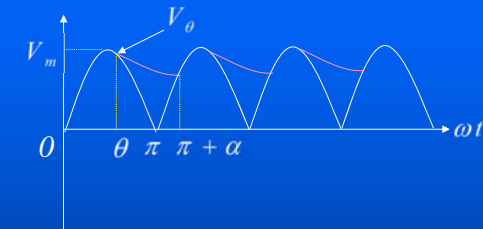

$$V_o(\omega t) = \begin{cases} V_m \sin \omega t & \text{at diode on} \\ (V_m \sin \theta) e^{-\frac{(\omega t - \theta)}{\omega RC}} & \text{at diode off} \end{cases}$$

$$* \quad V_\theta = V_m \sin \theta, \quad \theta = \tan^{-1}(-R \cdot \omega C)$$

4.2

: R-C

■ (Firing Angle)

for $\omega t = \alpha$


$$V_m \sin(\pi + \alpha) = (V_m \sin \theta) e^{-\frac{(\pi + \alpha - \theta)}{\omega RC}}$$

■ α

(Numerical Analysis)

- Pspice

4-5 L-C

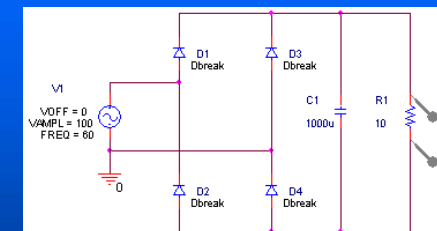


■ Parameter

- ✓ $R=10 \Omega$
- ✓ $L=5 \text{ mH}$
- ✓ $C=1000 \mu\text{F}$
- ✓ $f=60 \text{ Hz}$
- ✓ $V_m=100 \text{ V}$
- ✓ Transient Step
=0.50 ms


■ Find

- ✓ V

4.3

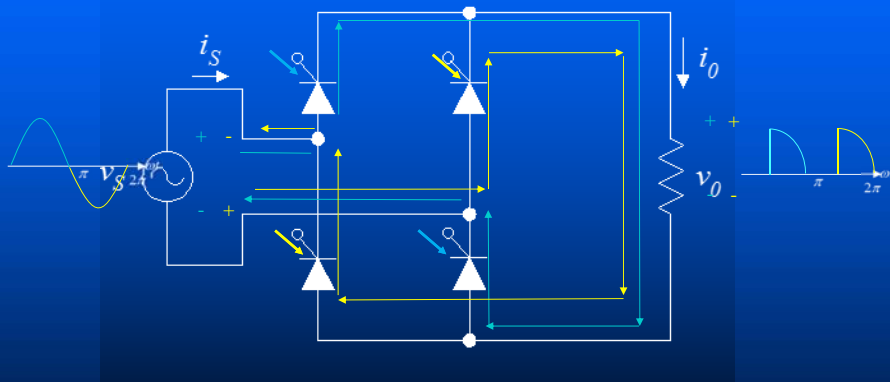

4.3

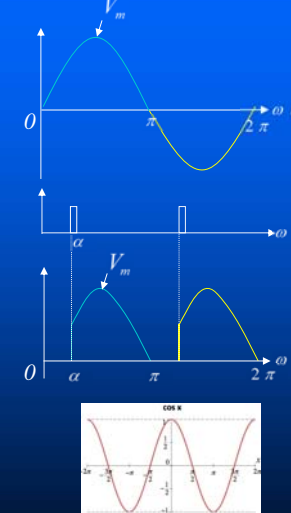

$$V_0 = \frac{1}{T} \int_{t_0}^{t_0+T} v(t) dt$$


$$V_0 = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$

$$\int \sin dt = -\cos t$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$= \frac{V_m}{\pi} (1 + \cos \alpha)$$

4.3

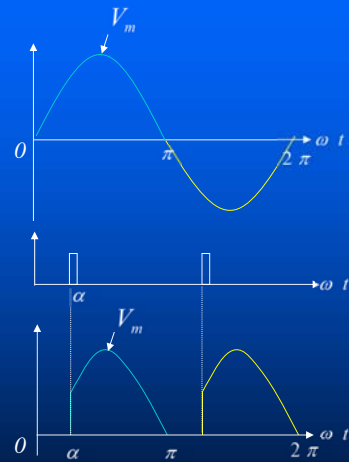

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t)}$$


$$\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2}$$

$$= \sqrt{\frac{V_m^2}{\pi} \left[\frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right]_{\alpha}^{\pi}}$$

$$= \sqrt{\frac{V_m^2}{\pi} \left(\frac{\pi}{2} - \frac{\sin 2\pi}{4} - \frac{\alpha}{2} + \frac{\sin 2\alpha}{4} \right)}$$

$$= V_m \sqrt{\left(\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi} \right)}$$

4-9

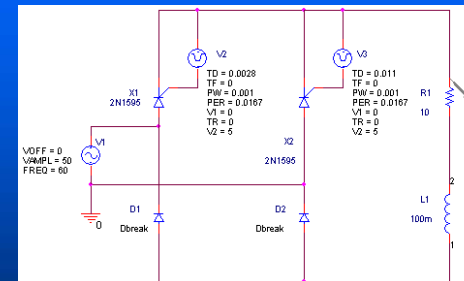


Parameter

- ✓ $R=10 \Omega$
- ✓ $L=100 \text{ mH}$
- ✓ $f=60 \text{ Hz}$
- ✓ $\alpha=60$
 - $TD1:0.0028(1/360)$
 - $TD2:0.011(4/360)$
- ✓ $V_m=169.7 \text{ V} \rightarrow 50 \text{ V}$
- ✓ Transient Step
=0.50 ms


Find: i, i_{avg}, P

4.4 3

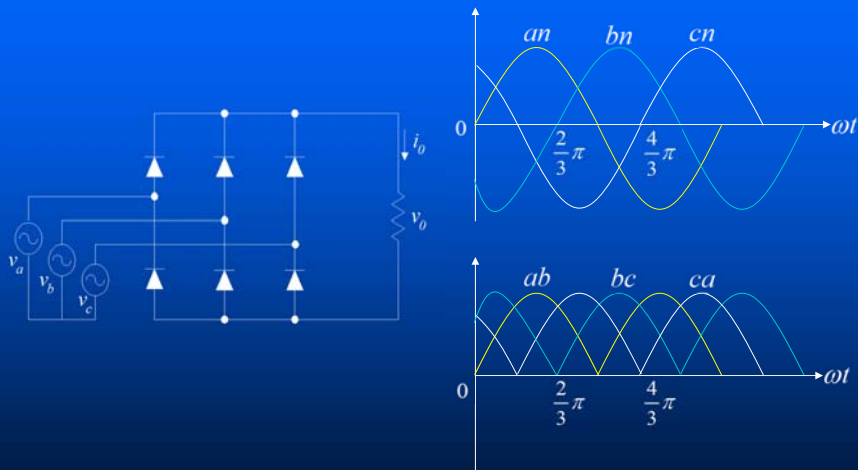

4.4 3

:

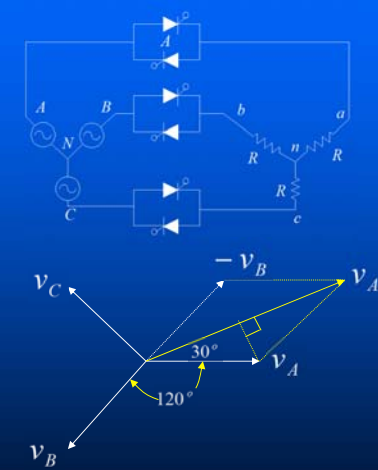

$$v_A = \sqrt{2}V \sin \omega t$$

$$v_B = \sqrt{2}V \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$v_C = \sqrt{2}V \sin \left(\omega t - \frac{4\pi}{3} \right)$$

$$v_{AB} = 2v_A \cos(30^\circ) \angle 30^\circ$$

$$= 2v_A \frac{\sqrt{3}}{2} \angle 30^\circ$$

$$= \sqrt{3}v_A \angle 30^\circ$$

3

결선	선간전류	선전류	전력
Y	$\sqrt{3} \times$ 상전압	상전류	$\sqrt{3} \times$ 상전압 \times 상전류
Δ	상전압	$\sqrt{3} \times$ 상전류	$\sqrt{3} \times$ 상전압 \times 상전류

4.4 3

: Fourier

$$V_0(t) = V_0 + \sum_{n=6,12,18} V_n \cos(n\omega_0 t + \pi)$$

$$V_0 = \frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} V_{m,L-L} \sin \omega t d(\omega t) = \frac{V_{m,L-L}}{\pi/3} \left[-\cos \omega t \right]_{\pi/3}^{2\pi/3}$$

$$= \frac{V_{m,L-L}}{\pi/3} \left\{ -\cos \frac{2\pi}{3} + \cos \frac{\pi}{3} \right\} = \frac{V_{m,L-L}}{\pi/3} \left\{ -\left(-\frac{1}{2}\right) + \frac{1}{2} \right\}$$

$$= \frac{3V_{m,L-L}}{\pi} = 0.95V_{m,L-L}$$

$$V_n = \frac{V_l}{\pi(n^2 - 1)}, \quad n = 6, 12, 18$$


4.4 3 :

■

$$i_a(t) = \frac{2\sqrt{3}}{\pi} I_0 (\cos \omega_0 t - \frac{1}{5} \cos 5\omega_0 t + \frac{1}{7} \cos 7\omega_0 t - \dots)$$

■

- Filter

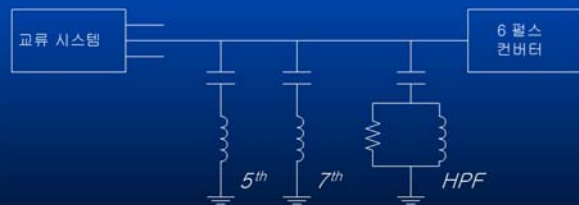

4-12 3 (1)



(a)

$$V_0 = \frac{3V_{m,L-L}}{\pi} = \frac{3\sqrt{2}(480)}{\pi} = 648V$$

(b)


$$I_0 = \frac{V_0}{R} = \frac{648}{25} = 25.9 A$$

(c)

$$I_{D,avg} = \frac{I_0}{3} = \frac{25.9}{3} = 8.63 A$$

$$I_{D,rms} = \frac{I_{0,rms}}{\sqrt{3}} \approx \frac{25.9}{\sqrt{3}} = 15.0 A$$

4-12 3 (2)

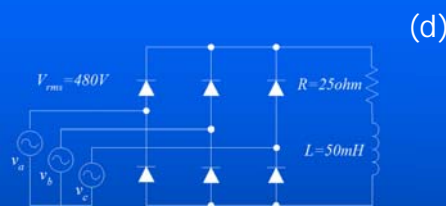


(d)

$$I_{s,avg} = \sqrt{\frac{2}{3}} I_{0,rms} \\ \approx \sqrt{\frac{2}{3}} (25.9) = 21.2 A$$

(e)

$$S = \sqrt{3} V_{L-L,rms} I_{0,rms} \\ = \sqrt{3} (480) (21.2) \\ = 17.6 KVA$$

4-12 3 : Pspice Simulation

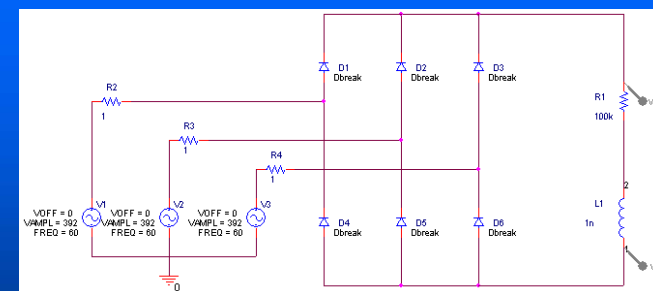


■ Parameter

$$R = 100 k\Omega \quad L = 50 mH \quad f = 60 Hz$$

$$V_m = \frac{\sqrt{2}(480)}{\sqrt{3}} = 392 \quad Step = 0:0.1 ms:50 ms$$

■ Find : V_0, I_{avg}, I_{rms}

4.5.3

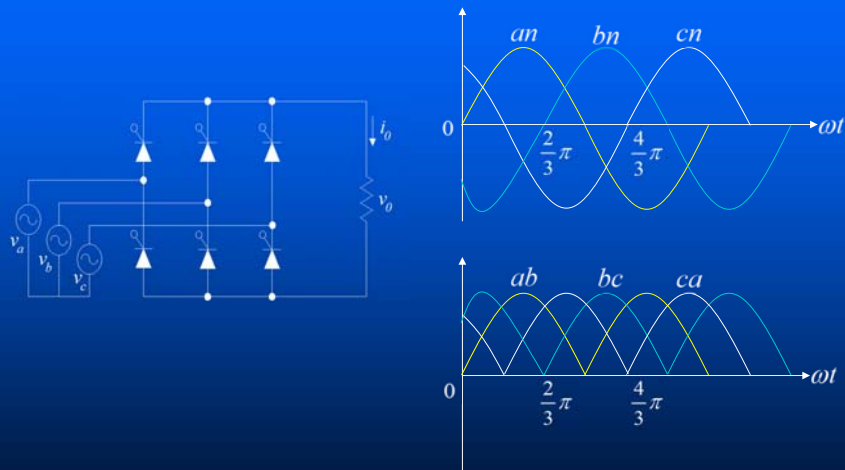

4.5.2.3

$$\begin{aligned}
 V_0 &= \frac{1}{\pi/3} \int_{\frac{\pi}{3}+\alpha}^{\frac{2\pi}{3}+\alpha} V_{m,L-L} \sin \omega t d(\omega t) \\
 &= \frac{V_{m,L-L}}{\pi/3} \left[-\cos \omega t \right]_{\frac{\pi}{3}+\alpha}^{\frac{2\pi}{3}+\alpha} \\
 &= \frac{V_{m,L-L}}{\pi/3} \left\{ -\cos \left(\frac{2\pi}{3} + \alpha \right) + \cos \left(\frac{\pi}{3} + \alpha \right) \right\} \quad \boxed{\cos \frac{2\pi}{3} = -\cos \frac{\pi}{3}} \\
 &= \frac{V_{m,L-L}}{\pi/3} \left\{ \cos \left(\frac{\pi}{3} - \alpha \right) + \cos \left(\frac{\pi}{3} + \alpha \right) \right\} \quad \boxed{\begin{aligned} \cos(x+y) &= \cos x \cos y - \sin x \sin y \\ \cos(x-y) &= \cos x \cos y + \sin x \sin y \end{aligned}} \\
 &= \frac{V_{m,L-L}}{\pi/3} \left\{ \cos \frac{\pi}{3} \cos \alpha + \sin \frac{\pi}{3} \sin \alpha + \cos \frac{\pi}{3} \cos \alpha - \sin \frac{\pi}{3} \sin \alpha \right\} \\
 &= \frac{3V_{m,L-L}}{\pi} 2 \cos \frac{\pi}{3} \cos \alpha = \frac{3V_{m,L-L}}{\pi} \cos \alpha
 \end{aligned}$$

4.5.2.3 (2)

■

$$V_0 = \frac{1}{\pi/3} \int_{\frac{\pi}{3}+\alpha}^{\frac{2\pi}{3}+\alpha} V_l \sin \omega t d(\omega t) = \frac{3V_l}{\pi} \cos \alpha$$

■ 12 Pulse

$$V_0 = V_{0Y} + V_{0\Delta} = \frac{6V_l}{\pi} \cos \alpha$$

■ 12 Pulse

$$i_{ac}(t) = i_Y(t) + i_{\Delta}(t) = \frac{4\sqrt{3}}{\pi} \left(\cos \omega_0 t - \frac{1}{11} \cos 11\omega_0 t + \dots \right)$$

4.6

